

Example #17: When a 6.0 V EMF battery was connected to a 15 Ω resistance, a current of 375 mA occurred and the voltmeter reading was 5.625 V.

(a) Find the internal resistance r of this supply.

(b) If this battery is now connected to a 5.0 Ω resistor, what current will flow?

$$a) \quad V_T = \mathcal{E} - Ir \quad \text{where } V_T = \text{voltmeter reading}$$

$$5.625 = 6.0 - .375 r$$

$$\boxed{r = 1.0 \Omega}$$

$$b) \quad R_o = 5.0 \Omega$$

$$V_T = \mathcal{E} - Ir \quad \text{and} \quad V_T = IR_o$$

$$\text{so } IR_o = \mathcal{E} - Ir \Rightarrow \mathcal{E} = IR_o + Ir$$

$$\rightarrow I = \frac{\mathcal{E}}{R_o + r} = \frac{6}{5 + 1}$$

$$\boxed{I = 1.0 \text{ A}}$$